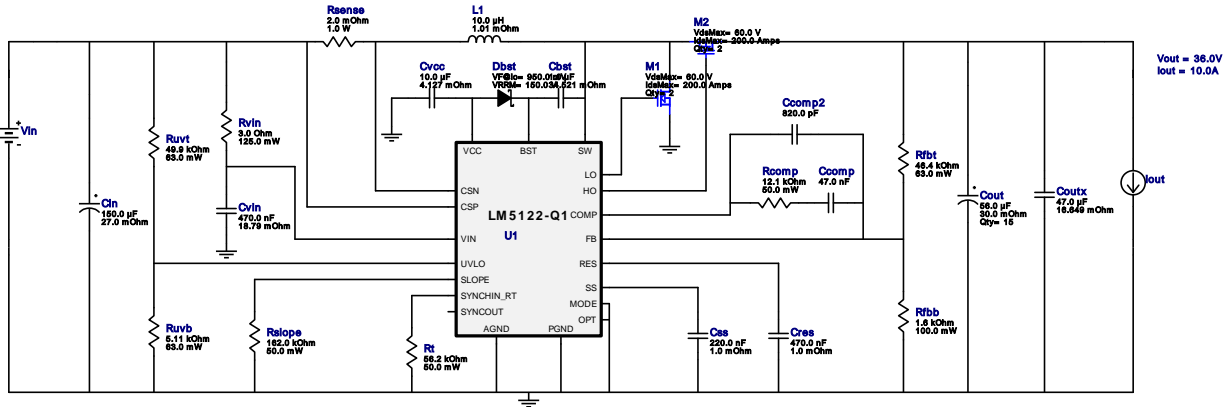


WEBENCH® Design Report

Design : 5 LM5122QMH/NOPB
LM5122QMH/NOPB 15V-22V to 36.00V @ 10A

VinMin = 15.0V
VinMax = 22.0V
Vout = 36.0V
Iout = 10.0A

Device = LM5122QMH/NOPB
Topology = Boost
Created = 2026-01-17 05:07:51.755
BOM Cost = \$40.82
BOM Count = 40
Total Pd = 9.25W



1. This regulator device is qualified for Automotive applications. All passives and other components selected in this design may not be qualified for Automotive applications. The user is required to verify that all components in the design meet the qualification and safety requirements for their specific application. View WEBENCH(R) Disclaimer.

Design Alerts







Component Selection Information







The LM5122-Q1 is qualified for Automotive applications. All passives and other components selected in this design may not be qualified for Automotive applications. The user is required to verify that all components in the design meet the qualification and safety requirements for their specific application.







Electrical BOM







Name	Manufacturer	Part Number	Properties	Qty	Price	Footprint
Cbst	Taiyo Yuden	MSASU21GSB7105KTNA01 Series= X7R	Cap= 1.0 uF ESR= 34.521 mOhm VDC= 50.0 V IRMS= 1.26652 A	1	\$0.04	 0805 7 mm ²
Ccomp	Kemet	C0805C473J3GACTU Series= C0G/NP0	Cap= 47.0 nF VDC= 25.0 V IRMS= 0.0 A	1	\$0.21	 0805 7 mm ²
Ccomp2	Samsung Electro-Mechanics	CL05C821JB5NNNC Series= C0G/NP0	Cap= 820.0 pF VDC= 50.0 V IRMS= 0.0 A	1	\$0.01	 0402 3 mm ²
Cin	Panasonic	EEHZA1V151P Series= ZA	Cap= 150.0 uF ESR= 27.0 mOhm VDC= 35.0 V IRMS= 2.3 A	1	\$1.15	 SM_RADIAL_8MM 113 mm ²
Cout	Panasonic	EEHZA1J560P Series= ZA	Cap= 56.0 uF ESR= 30.0 mOhm VDC= 63.0 V IRMS= 1.8 A	15	\$0.93	 Panasonic_G 151 mm ²
Coutx	TDK	CKG57NX7R1H476M500JH Series= X7R	Cap= 47.0 uF ESR= 16.649 mOhm VDC= 50.0 V IRMS= 0.0 A	1	\$5.07	 2220 54 mm ²
Cres	Taiyo Yuden	TMK212BJ474KD-T Series= X5R	Cap= 470.0 nF ESR= 1.0 mOhm VDC= 20.0 V IRMS= 0.0 A	1	\$0.02	 0805 7 mm ²


Name	Manufacturer	Part Number	Properties	Qty	Price	Footprint
Css	MuRata	GRM155R61A224KE19D Series= X5R	Cap= 220.0 nF ESR= 1.0 mOhm VDC= 10.0 V IRMS= 0.0 A	1	\$0.01	 0402 3 mm²
Cvcc	MuRata	GRM21BR61C106KE15L Series= X5R	Cap= 10.0 uF ESR= 4.127 mOhm VDC= 16.0 V IRMS= 2.46634 A	1	\$0.03	 0805 7 mm²
Cvin	TDK	C1005X5R1V474K050BC Series= X5R	Cap= 470.0 nF ESR= 18.79 mOhm VDC= 35.0 V IRMS= 0.0 A	1	\$0.02	 0402 3 mm²
Dbst	SMC Diode Solutions	SK215ATR	VF@Io= 950.0 mV VRRM= 150.0 V	1	\$0.06	 SMA 37 mm²
L1	Würth Elektronik	7843763540100	L= 10.0 µH 1.01 mOhm	1	\$15.05	 WE-HCFAT_3540 1634 mm²
M1	Texas Instruments	CSD18540Q5B	VdsMax= 60.0 V IdsMax= 200.0 Amps	2	\$0.75	 DNK0008A 56 mm²
M2	Texas Instruments	CSD18533Q5A	VdsMax= 60.0 V IdsMax= 200.0 Amps	2	\$0.33	 DQJ0008A 55 mm²
Rcomp	Yageo	RC0201FR-0712K1L Series= ?	Res= 12.1 kOhm Power= 50.0 mW Tolerance= 1.0%	1	\$0.01	 0201 2 mm²
Rfbb	Yageo	RC0603FR-071K6L Series= ?	Res= 1.6 kOhm Power= 100.0 mW Tolerance= 1.0%	1	\$0.01	 0603 5 mm²
Rfbt	Vishay-Dale	CRCW040246K4FKED Series= CRCW..e3	Res= 46.4 kOhm Power= 63.0 mW Tolerance= 1.0%	1	\$0.01	 0402 3 mm²
Rsense	Stackpole Electronics Inc	CSNL1206FT2L00 Series= CSNL	Res= 2.0 mOhm Power= 1.0 W Tolerance= 1.0%	1	\$0.19	 1206 11 mm²
Rslope	Yageo	RC0201FR-07162KL Series= ?	Res= 162.0 kOhm Power= 50.0 mW Tolerance= 1.0%	1	\$0.01	 0201 2 mm²
Rt	Yageo	RC0201FR-0756K2L Series= ?	Res= 56.2 kOhm Power= 50.0 mW Tolerance= 1.0%	1	\$0.01	 0201 2 mm²
Ruvb	Vishay-Dale	CRCW04025K11FKED Series= CRCW..e3	Res= 5.11 kOhm Power= 63.0 mW Tolerance= 1.0%	1	\$0.01	 0402 3 mm²
Rvvt	Vishay-Dale	CRCW040249K9FKED Series= CRCW..e3	Res= 49.9 kOhm Power= 63.0 mW Tolerance= 1.0%	1	\$0.01	 0402 3 mm²
Rvin	Yageo	RC0805FR-073RL Series= ?	Res= 3.0 Ohm Power= 125.0 mW Tolerance= 1.0%	1	\$0.01	 0805 7 mm²
U1	Texas Instruments	LM5122QMH/NOPB	Switcher	1	\$2.76	 MXA20A 71 mm²

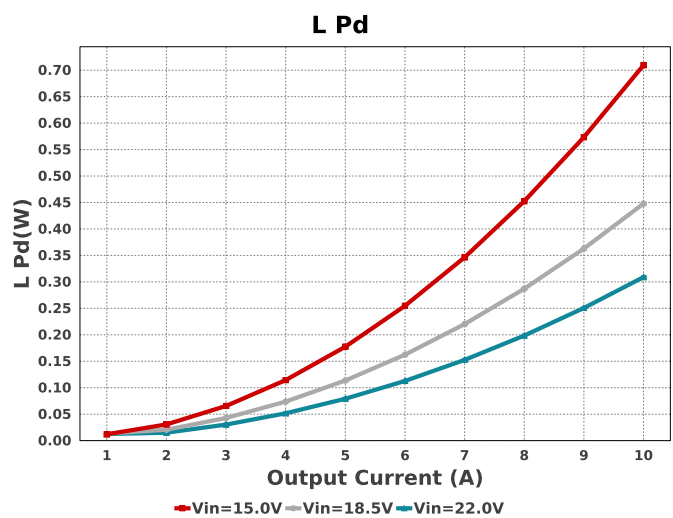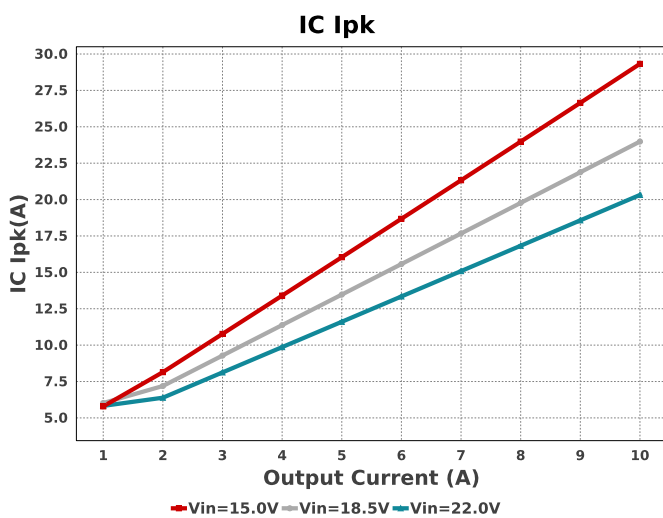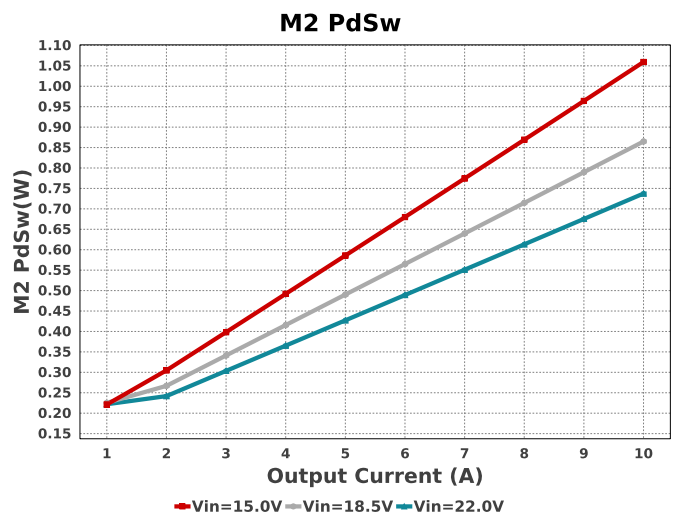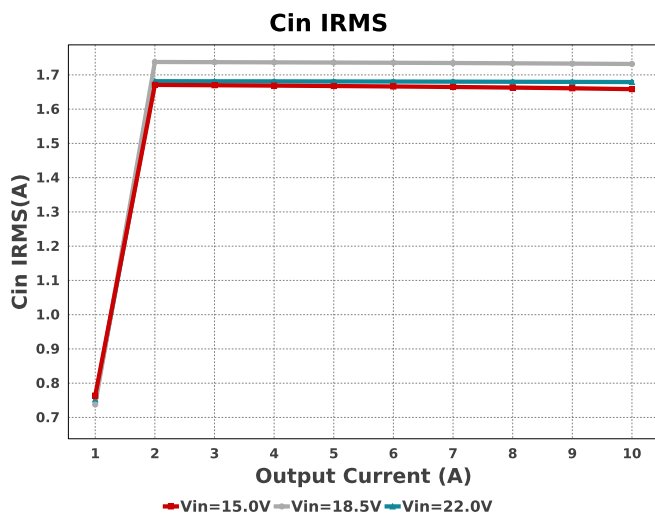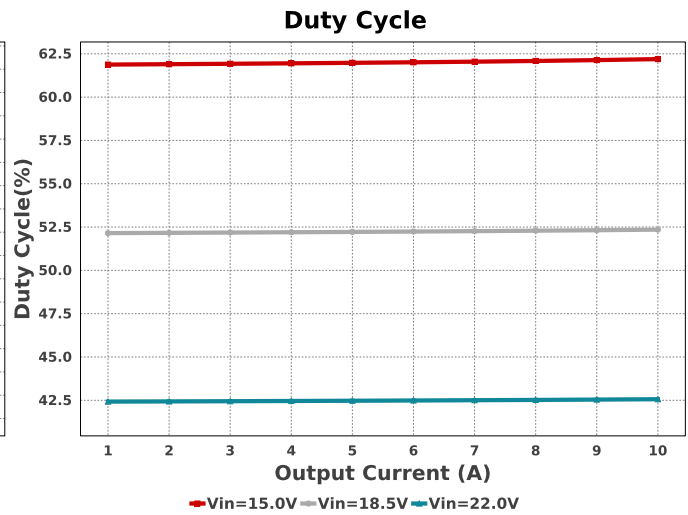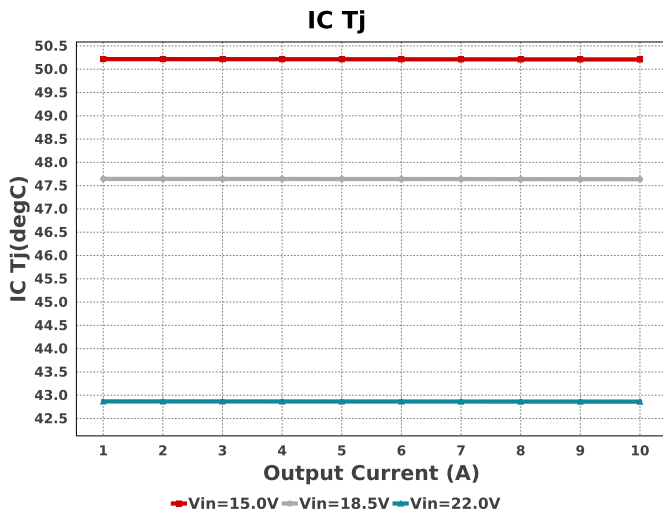

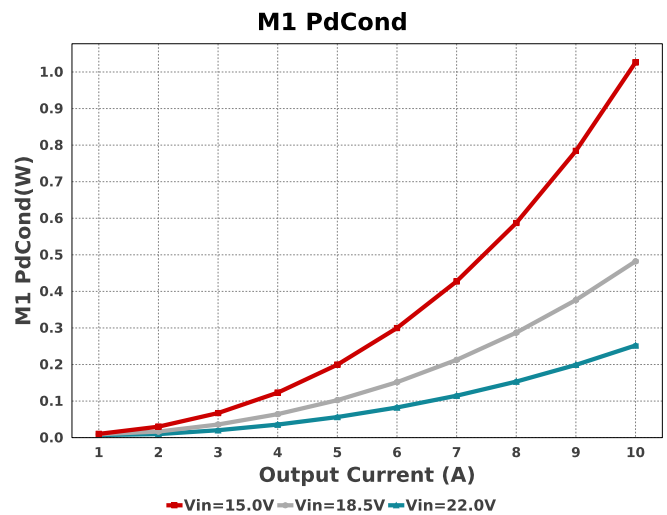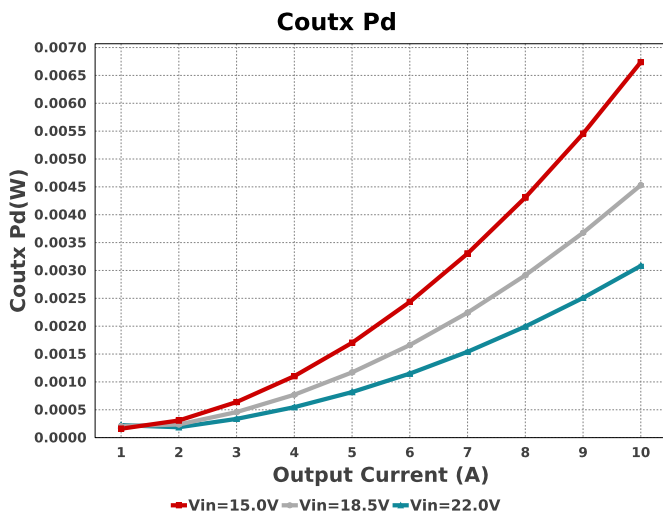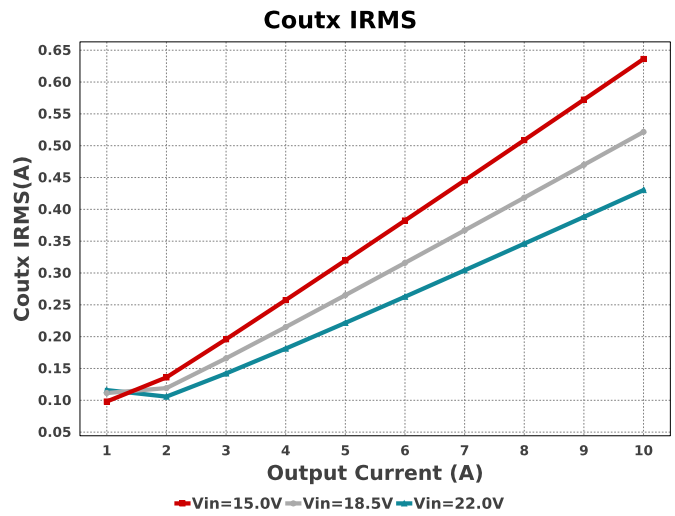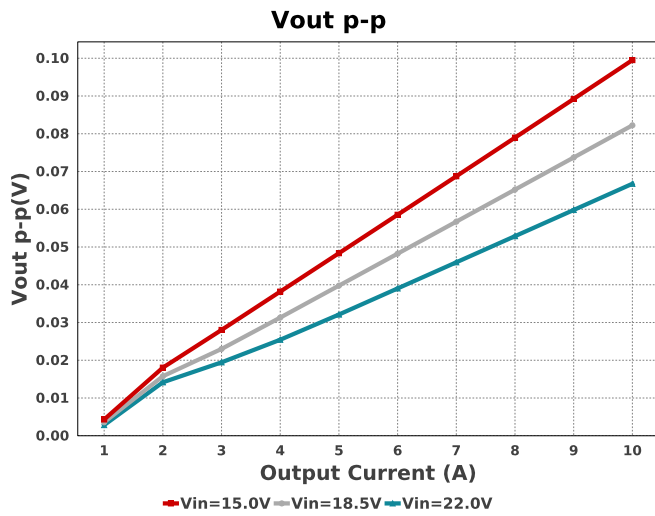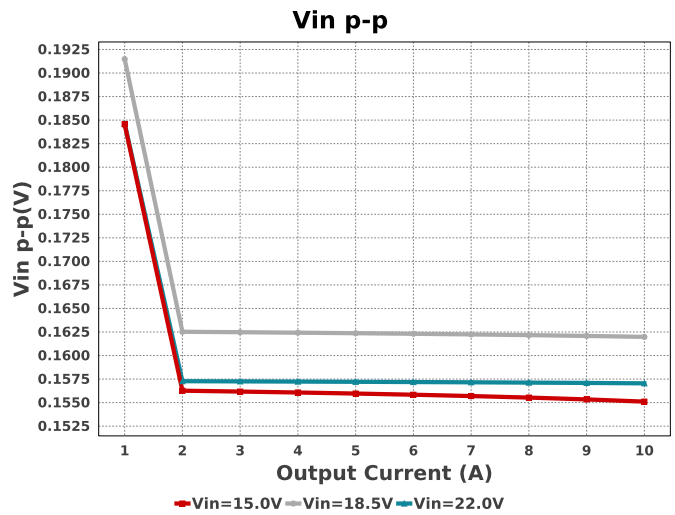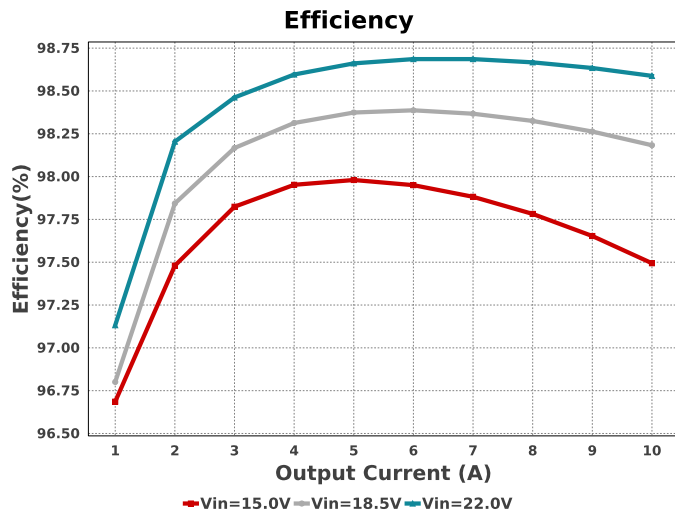

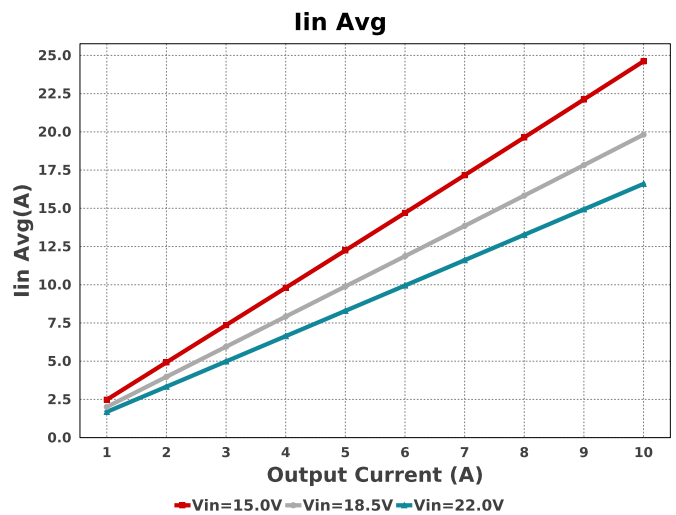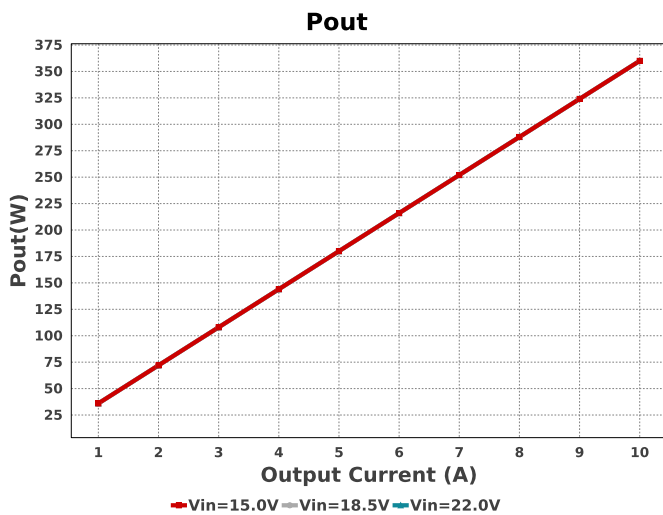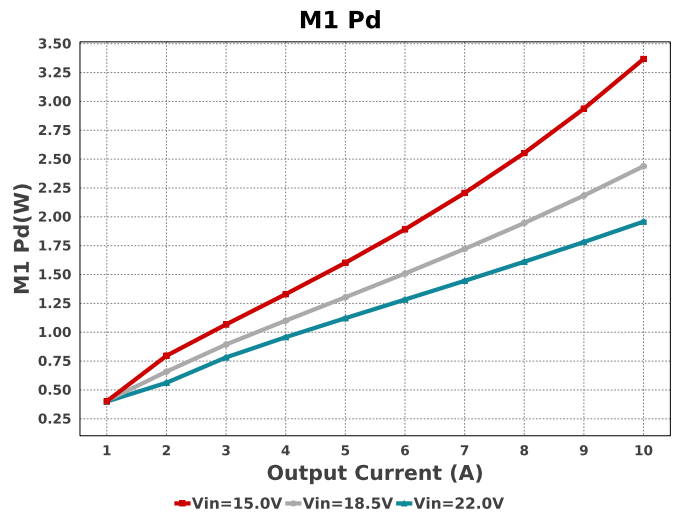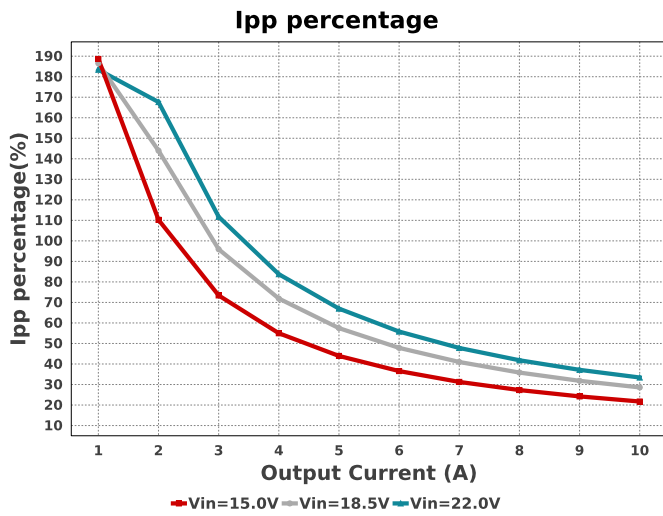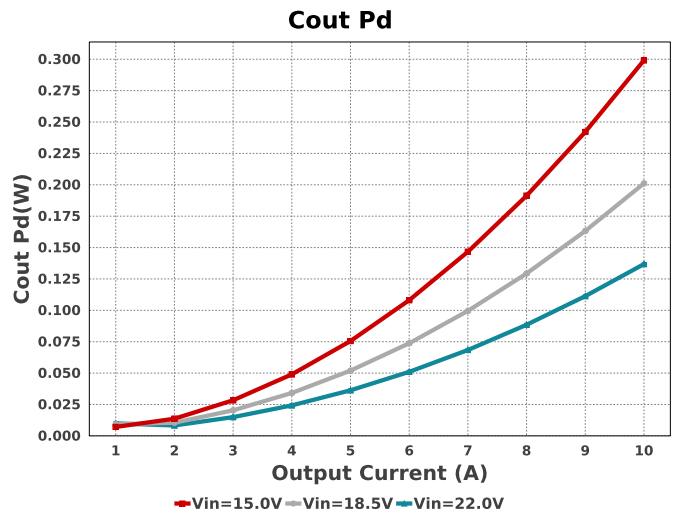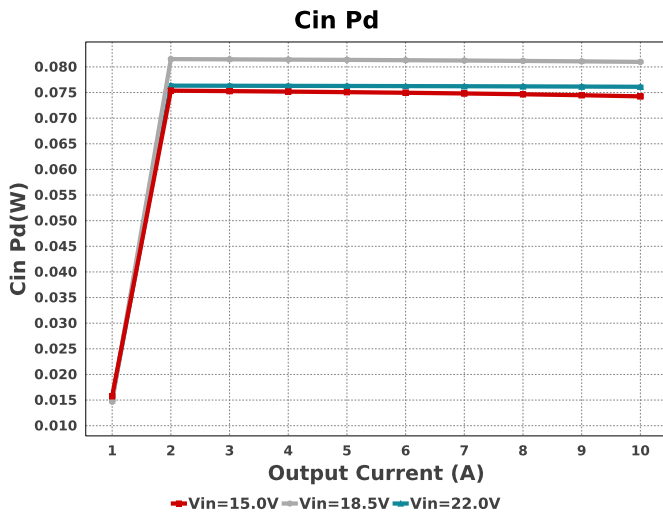

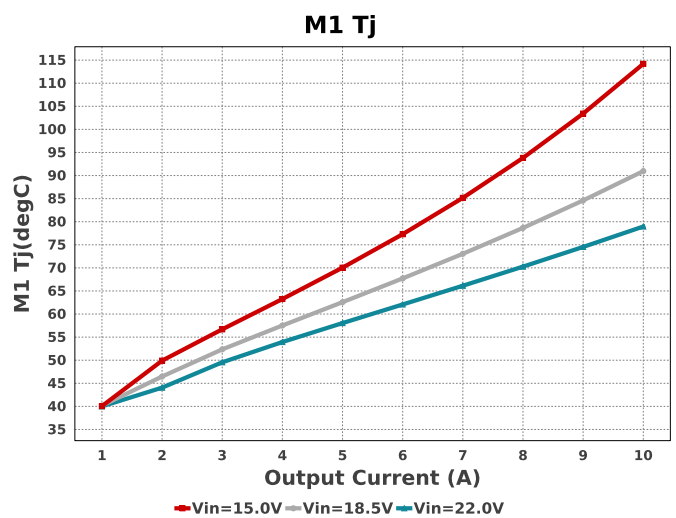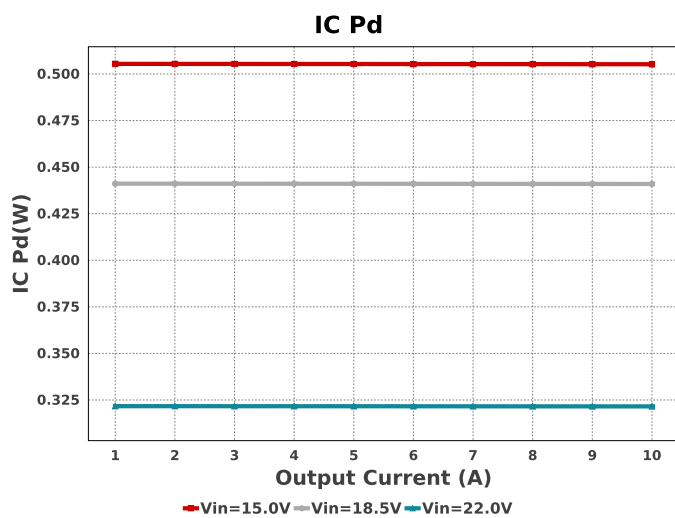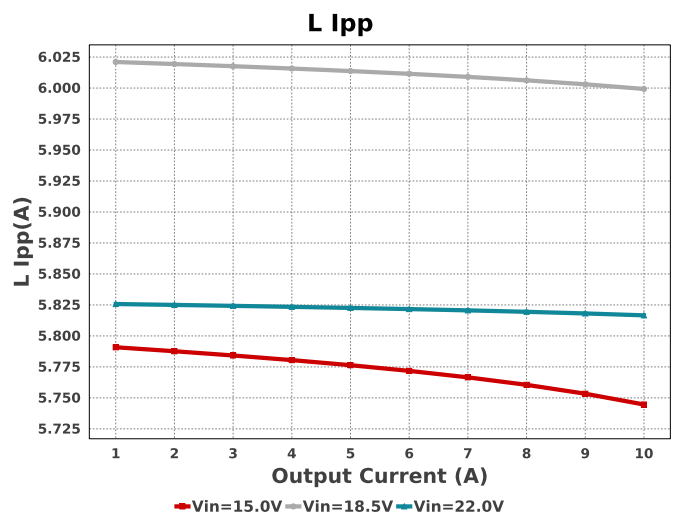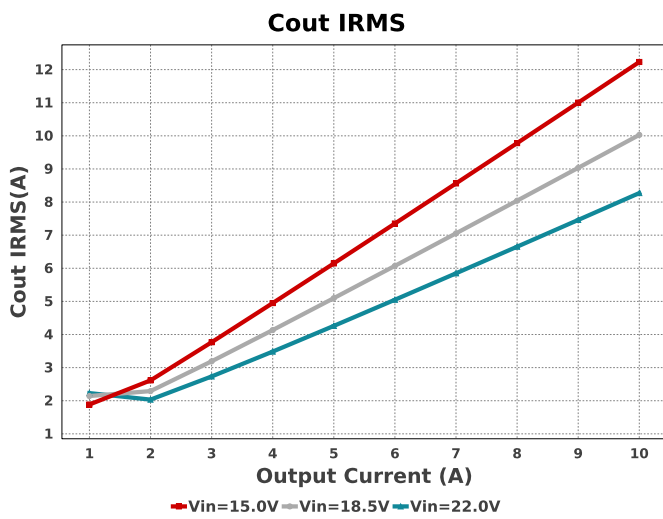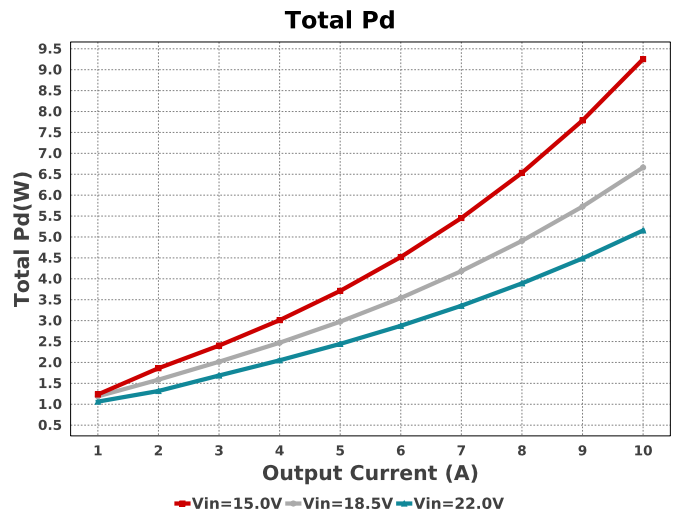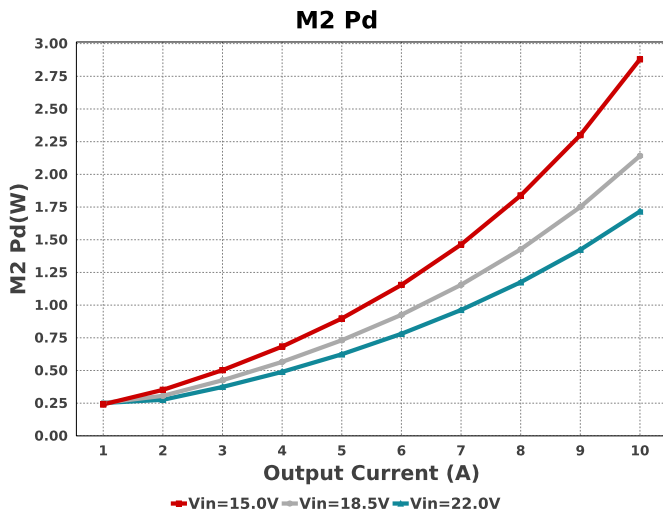

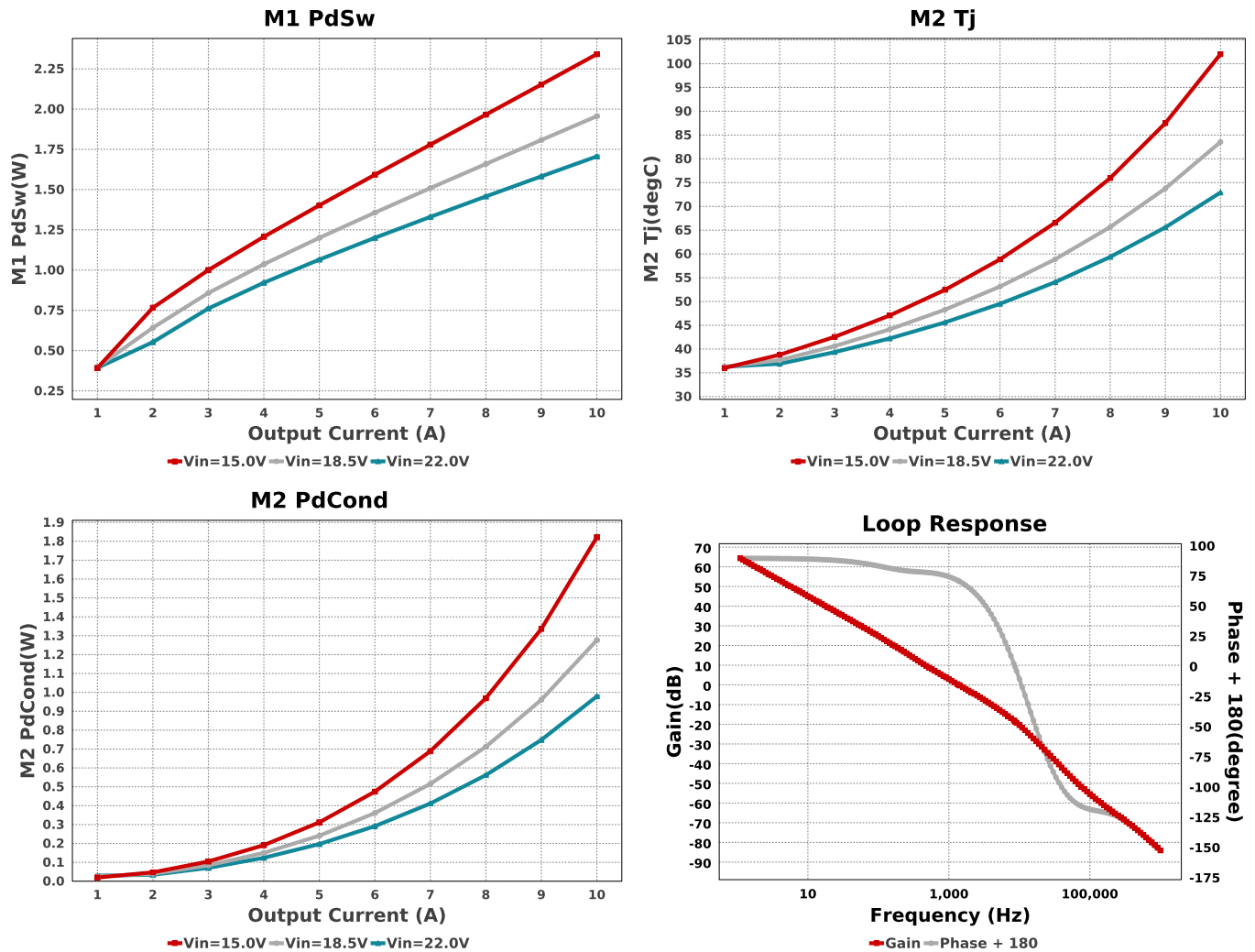

Operating Values

#	Name	Value	Category	Description
1.	Cin IRMS	1.658 A	Capacitor	Input capacitor RMS ripple current
2.	Cin Pd	74.252 mW	Capacitor	Input capacitor power dissipation
3.	Cout IRMS	12.23 A	Capacitor	Output capacitor RMS ripple current
4.	Cout Pd	299.16 mW	Capacitor	Output capacitor power dissipation
5.	Coutx IRMS	636.222 mA	Capacitor	Output capacitor_x RMS ripple current
6.	Coutx Pd	6.739 mW	Capacitor	Output capacitor_x power loss
7.	IC Ipk	29.323 A	IC	Peak switch current in IC
8.	IC Pd	505.23 mW	IC	IC power dissipation
9.	IC Tj	50.209 degC	IC	IC junction temperature
10.	IC Tolerance	18.0 mV	IC	IC Feedback Tolerance
11.	ICThetaJA	40.0 degC/W	IC	IC junction-to-ambient thermal resistance
12.	Iin Avg	24.617 A	IC	Average input current
13.	Ipp percentage	21.718 %	Inductor	Inductor ripple current percentage (with respect to average inductor current)
14.	L Ipp	5.745 A	Inductor	Peak-to-peak inductor ripple current
15.	L Pd	709.41 mW	Inductor	Inductor power dissipation
16.	M1 Pd	3.368 W	Mosfet	M1 MOSFET total power dissipation
17.	M1 PdCond	1.026 W	Mosfet	M1 MOSFET conduction losses
18.	M1 PdSw	2.341 W	Mosfet	M1 MOSFET switching losses
19.	M1 Tj	114.19 degC	Mosfet	M1 MOSFET junction temperature
20.	M2 Pd	2.88 W	Mosfet	M2 MOSFET total power dissipation
21.	M2 PdCond	1.821 W	Mosfet	M2 MOSFET conduction losses
22.	M2 PdSw	1.059 W	Mosfet	M2 MOSFET switching losses
23.	M2 Tj	102.01 degC	Mosfet	M2 MOSFET junction temperature
24.	Cin Pd	74.252 mW	Power	Input capacitor power dissipation
25.	Cout Pd	299.16 mW	Power	Output capacitor power dissipation
26.	Coutx Pd	6.739 mW	Power	Output capacitor_x power loss
27.	IC Pd	505.23 mW	Power	IC power dissipation
28.	L Pd	709.41 mW	Power	Inductor power dissipation
29.	M1 Pd	3.368 W	Power	M1 MOSFET total power dissipation
30.	M1 PdCond	1.026 W	Power	M1 MOSFET conduction losses
31.	M1 PdSw	2.341 W	Power	M1 MOSFET switching losses

#	Name	Value	Category	Description
32.	M2 Pd	2.88 W	Power	M2 MOSFET total power dissipation
33.	M2 PdCond	1.821 W	Power	M2 MOSFET conduction losses
34.	M2 PdSw	1.059 W	Power	M2 MOSFET switching losses
35.	Total Pd	9.246 W	Power	Total Power Dissipation
36.	BOM Count	40	System	Total Design BOM count
			Information	
37.	Cross Freq	938.838 Hz	System	Bode plot crossover frequency
			Information	
38.	Duty Cycle	62.194 %	System	Duty cycle
			Information	
39.	Efficiency	97.496 %	System	Steady state efficiency
			Information	
40.	FootPrint	4.475 k mm ²	System	Total Foot Print Area of BOM components
			Information	
41.	Frequency	160.142 kHz	System	Switching frequency
			Information	
42.	Gain Marg	-17.413 dB	System	Bode Plot Gain Margin
			Information	
43.	Iout	10.0 A	System	Iout operating point
			Information	
44.	Low Freq Gain	64.765 dB	System	Gain at 1Hz
			Information	
45.	Mode	CCM	System	Conduction Mode
			Information	
46.	Phase Marg	68.83 deg	System	Bode Plot Phase Margin
			Information	
47.	Pout	360.0 W	System	Total output power
			Information	
48.	Total BOM	\$40.82	System	Total BOM Cost
			Information	
49.	Vin	15.0 V	System	Vin operating point
			Information	
50.	Vin p-p	155.106 mV	System	Peak-to-peak input voltage
			Information	
51.	Vout	36.0 V	System	Operational Output Voltage
			Information	
52.	Vout Actual	36.0 V	System	Vout Actual calculated based on selected voltage divider resistors
			Information	
53.	Vout Tolerance	3.482 %	System	Vout Tolerance based on IC Tolerance (no load) and voltage divider resistors if applicable
			Information	
54.	Vout p-p	99.508 mV	System	Peak-to-peak output ripple voltage
			Information	

Design Inputs

Name	Value	Description
Iout	10.0	Maximum Output Current
SoftStart	10.0 ms	Soft Start Time (ms)
VinMax	22.0	Maximum input voltage
VinMin	15.0	Minimum input voltage
Vout	36.0	Output Voltage
base_pn	LM5122-Q1	Base Product Number
source	DC	Input Source Type
Ta	30.0	Ambient temperature
UserFsw	160.142 k	Customer Selected Frequency

WEBENCH® Assembly

Component Testing

Some published data on components in datasheets such as Capacitor ESR and Inductor DC resistance is based on conservative values that will guarantee that the components always exceed the specification. For design purposes it is usually better to work with typical values. Since this data is not always available it is a good practice to measure the Capacitance and ESR values of C_{in} and C_{out} , and the inductance and DC resistance of $L1$ before assembly of the board. Any large discrepancies in values should be electrically simulated in WEBENCH to check for instabilities and thermally simulated in WebTHERM to make sure critical temperatures are not exceeded.

Soldering Component to Board


If board assembly is done in house it is best to tack down one terminal of a component on the board then solder the other terminal. For surface mount parts with large tabs, such as the DPAK, the tab on the back of the package should be pre-tinned with solder, then tacked into place by one of the pins. To solder the tab town to the board place the iron down on the board while resting against the tab, heating both surfaces simultaneously. Apply light pressure to the top of the plastic case until the solder flows around the part and the part is flush with the PCB. If the solder is not flowing around the board you may need a higher wattage iron (generally 25W to 30W is enough).

Initial Startup of Circuit

It is best to initially power up the board by setting the input supply voltage to the lowest operating input voltage 15.0V and set the input supply's current limit to zero. With the input supply off connect up the input supply to V_{in} and GND. Connect a digital volt meter and a load if needed to set the minimum lout of the design from V_{out} and GND. Turn on the input supply and slowly turn up the current limit on the input supply. If the voltage starts to rise on the input supply continue increasing the input supply current limit while watching the output voltage. If the current increases on the input supply, but the voltage remains near zero, then there may be a short or a component misplaced on the board. Power down the board and visually inspect for solder bridges and recheck the diode and capacitor polarities. Once the power supply circuit is operational then more extensive testing may include full load testing, transient load and line tests to compare with simulation results.

Load Testing

The setup is the same as the initial startup, except that an additional digital voltmeter is connected between V_{in} and GND, a load is connected between V_{out} and GND and a current meter is connected in series between V_{out} and the load. The load must be able to handle at least rated output power + 50% (7.5 watts for this design). Ideally the load is supplied in the form of a variable load test unit. It can also be done in the form of suitably large power resistors. When using an oscilloscope to measure waveforms on the prototype board, the ground leads of the oscilloscope probes should be as short as possible and the area of the loop formed by the ground lead should be kept to a minimum. This will help reduce ground lead inductance and eliminate EMI noise that is not actually present in the circuit.

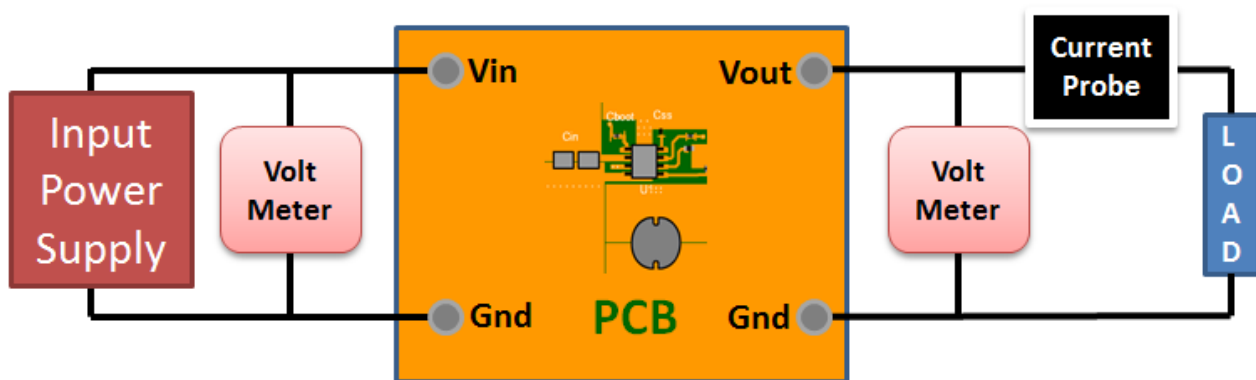

Design Assistance

1. The LM5122 is a wide range boost controller which is operable in an ultra wide input range of 4.5 to 65V. A boost regulator can maintain regulation for input voltages lower than the output voltage.
2. Feature Highlights: Automotive Qualified 12V to 14V V_{in} , 24V V_{out} , 2A as typical design input conditions
3. The LM5122-Q1 is qualified for Automotive applications. All passives and other components selected in this design may not be qualified for Automotive applications. The user is required to verify that all components in the design meet the qualification and safety requirements for their specific application
4. Master key : FF65EAF3001A9529E4D1AF68526A0C6D[v1]
5. **LM5122-Q1** Product Folder : <http://www.ti.com/product/LM5122%2DQ1> : contains the data sheet and other resources.

Important Notice and Disclaimer

TI provides technical and reliability data (including datasheets), design resources (including reference designs), application or other design advice, web tools, safety information, and other resources AS IS and with all faults, and disclaims all warranties. These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, or other requirements.

These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

Providing these resources does not expand or otherwise alter TI's applicable Terms of Sale or other applicable terms available either on ti.com or provided in conjunction with TI products.